



Analog-to-digital conversion Digital-to-analog conversion

Part 2

ECE 2534



Outline

- Motivation
- Basic idea
- ADC on the PIC32
- Digital-to-analog conversion methods
- Analog-to-digital conversion methods

REMINDER:

Need to interface with the real (analog) world



Analog to digital:

$$D = \left\lfloor \left(\frac{V_{In} - V_{RefLow}}{V_{RefHigh} - V_{RefLow}} \right) \times 2^n \right\rfloor$$

Digital to analog:

$$V_{Out} = \left(\frac{D}{2^n} \right) (V_{RefHigh} - V_{RefLow}) + V_{RefLow}$$



Outline

- Motivation
- Basic idea
- ADC on the PIC32
- **Digital-to-analog conversion methods**
- Analog-to-digital conversion methods



Digital-to-Analog Conversion

■ Goal

- **Convert a digital value to an analog voltage**
- Usually an unsigned binary number, 8 to 16 bits
- Common output range: a few volts, such as 0 to V_{cc} or -12 V to $+12\text{ V}$

■ Normally use a linear mapping

■ Common concerns


- Resolution
- Accuracy
- Conversion speed




Three methods for D/A conversion

- Binary weighted ladder
- R-2R ladder
- Pulse-width modulation


First. . . some op-amp circuits

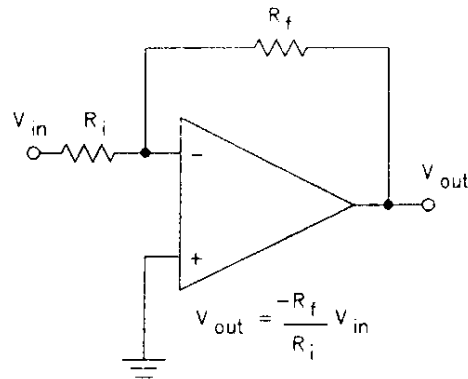


(a) Inverting Amplifier

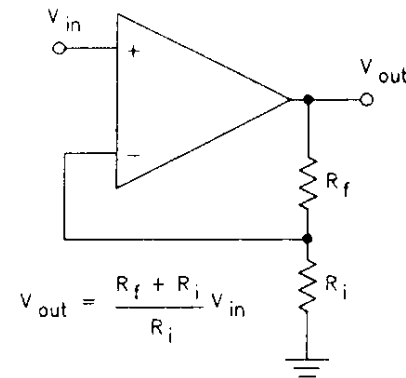

(b) Noninverting Amplifier

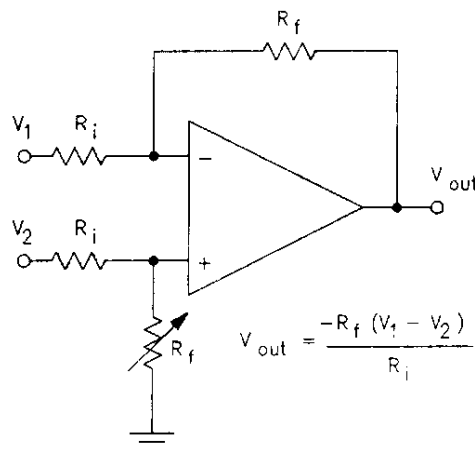


(c) Differential Amplifier

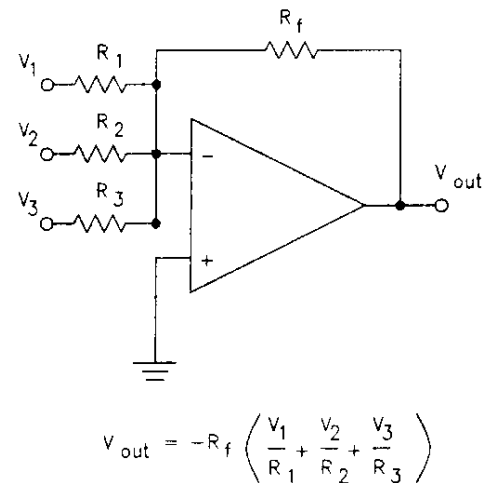

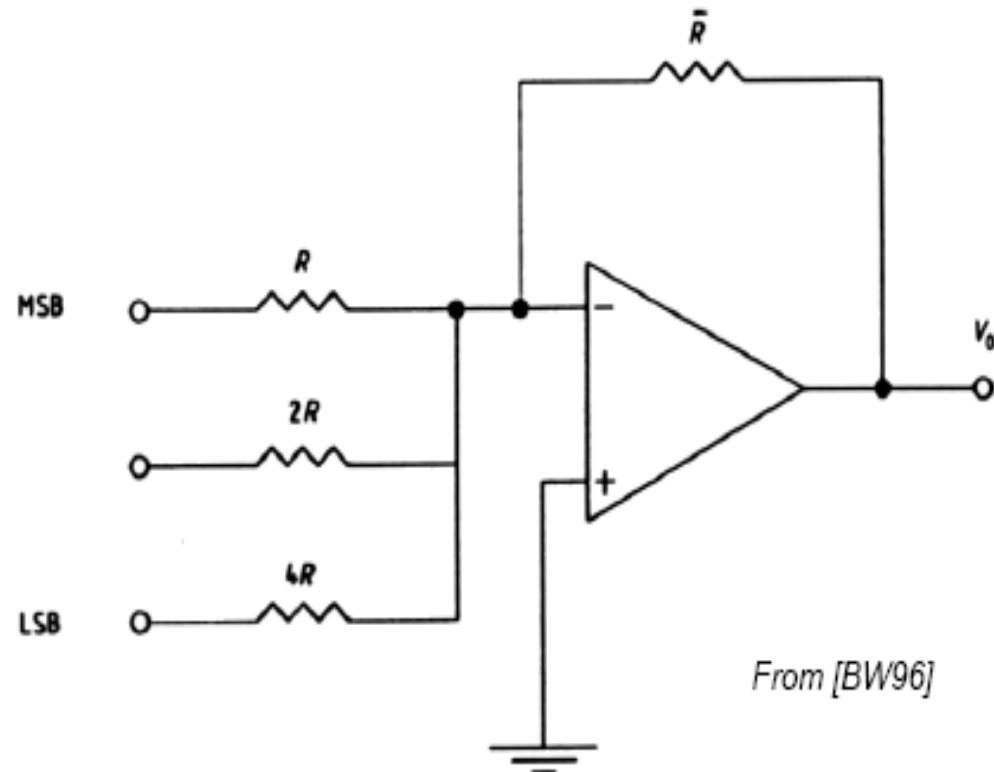(d) Summing Amplifier

Binary weighted ladder

- Based on the Summing Amplifier
- One bit per input
- Each input resistor is 2X the previous value
- $V_{RefHigh}$ if input bit is 1, otherwise ground
- 3-bit example:






Binary weighted ladder

- Fast conversion, *but* . . .
- Not practical for large n because many different high-accuracy resistors are needed
- The lowest-value resistor R affects the MSB and must have the highest accuracy
- “usually limited to 8-bit resolution or less”


R-2R ladder

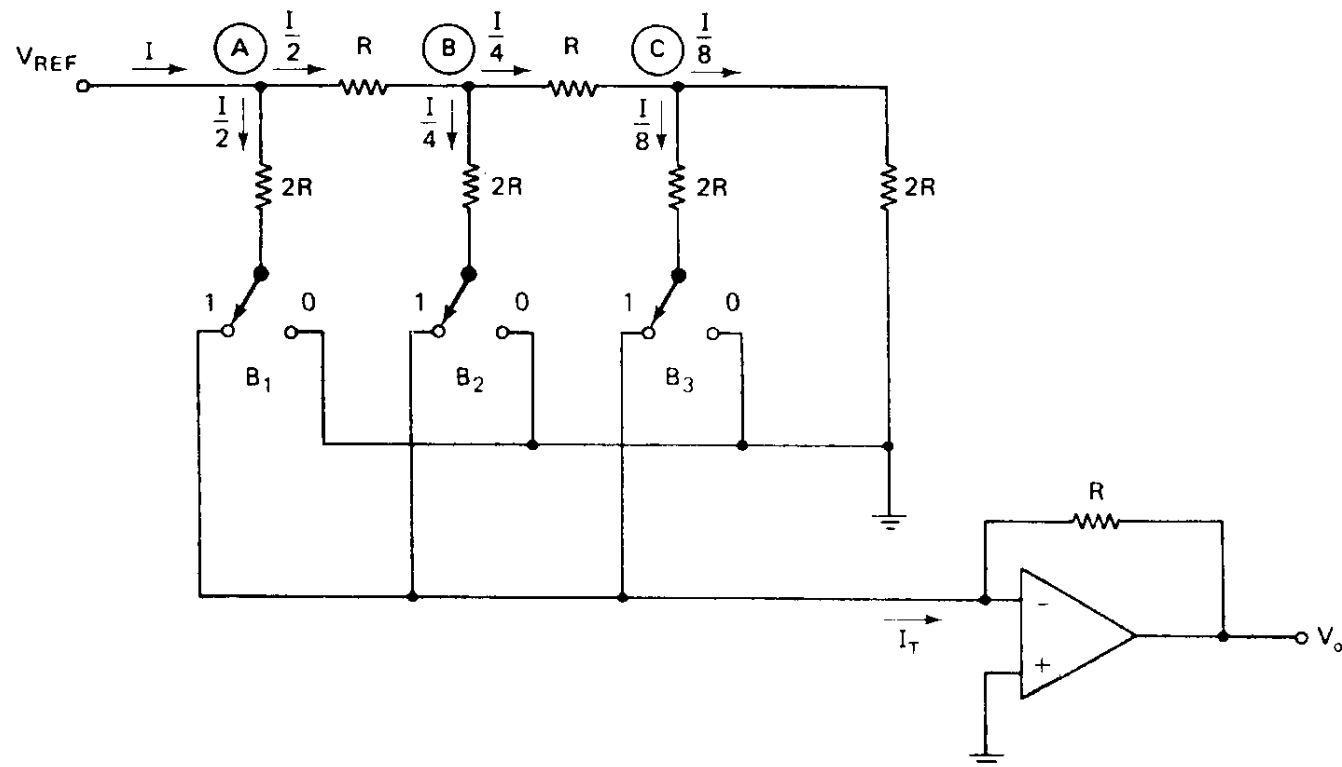- Uses $2n$ resistors, with only two resistance values
- Somewhat slower than the previous case, because the RC effects increase for each additional R-2R stage
- 3-bit example:



PWM technique

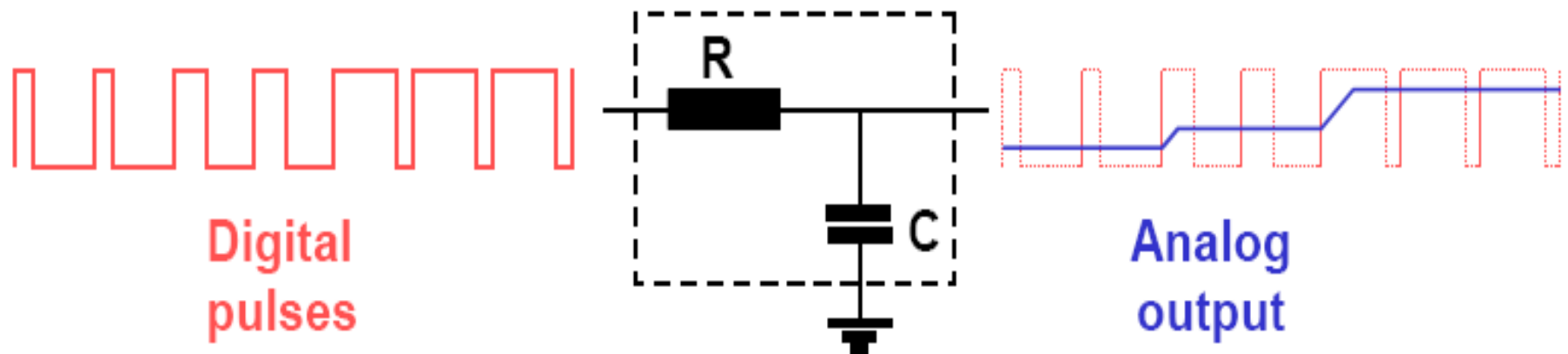- Simplest type of DAC
- Digital system generates a PWM waveform, selecting pulse widths based on the binary values being converted to analog form
- The waveform is input to a low-pass analog filter





PWM technique


- Often used for electric motor speed control
- Now becoming common in high-fidelity audio



Outline


- Motivation
- Basic idea
- ADC on the PIC32
- Digital-to-analog conversion methods
- **Analog-to-digital conversion methods**

System overview, again

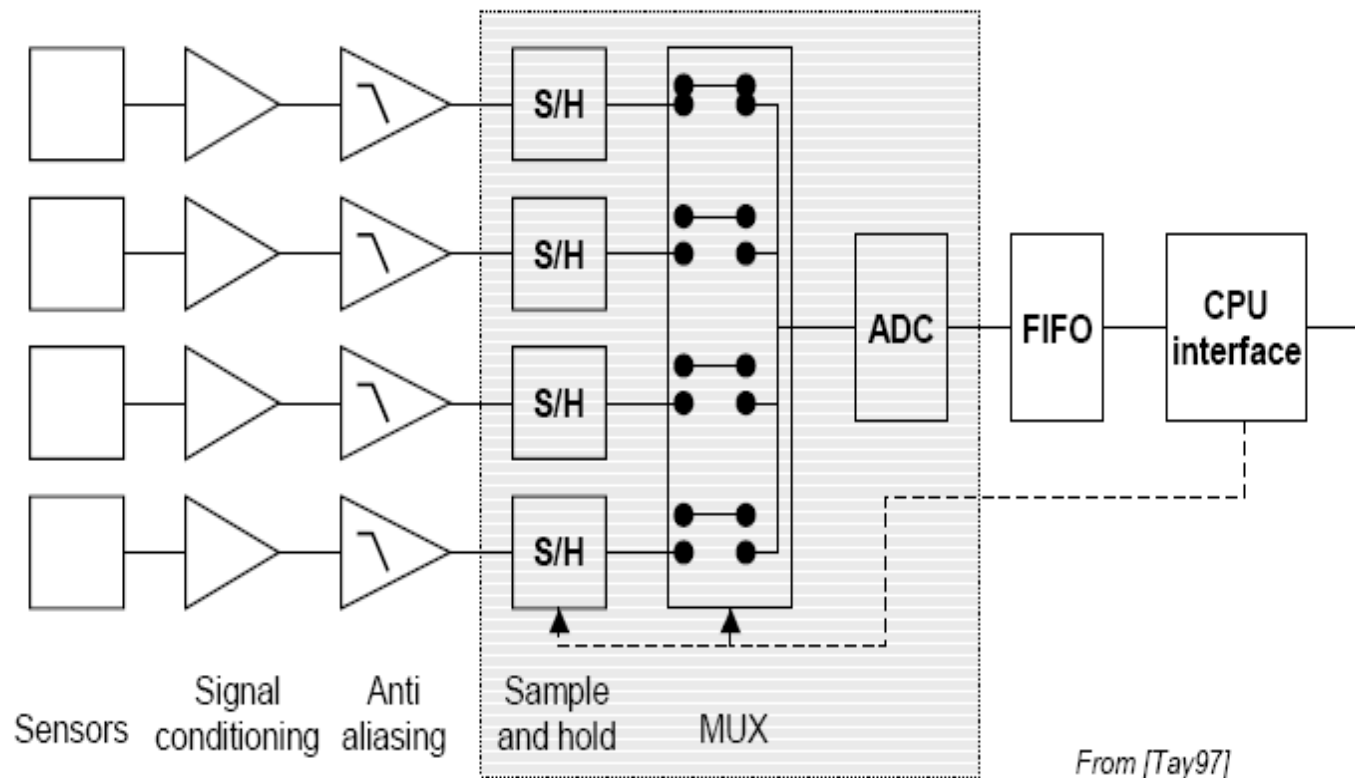

Comparison with PIC32

FIGURE 22-1: ADC1 MODULE BLOCK DIAGRAM

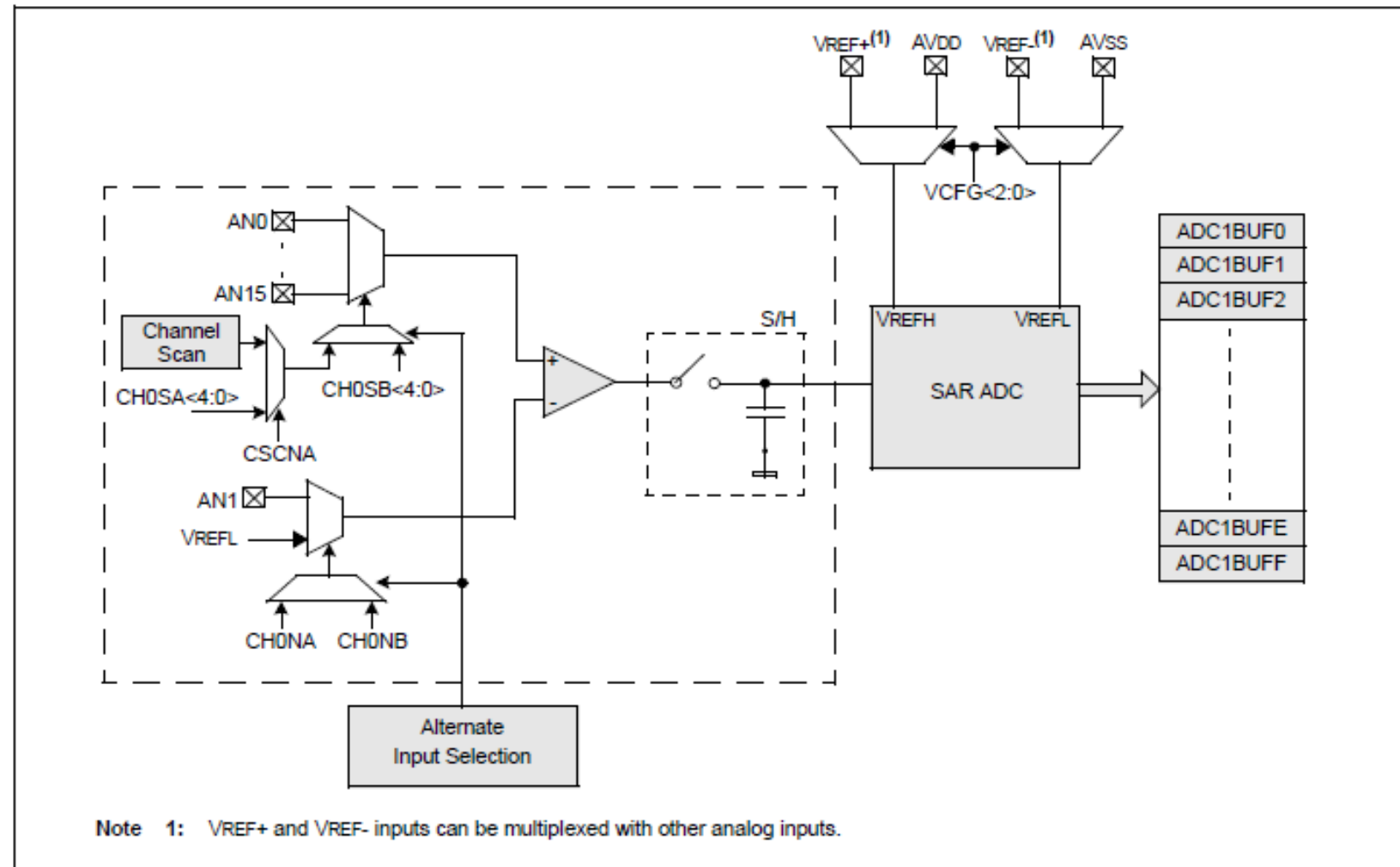



■ *Signal conditioning*

- Many sensors provide noisy, weak signals (e.g., a few mV or uV)
- Often need to amplify, filter, linearize

■ *Antialiasing*

- For time-varying signals, often use LPF to make sure the Nyquist criterion is satisfied


Sample and hold circuits

■ *Two basic operating modes*

- **Sample mode:** The S/H output follows the input (“Acquisition time”)
- **Hold mode:** Try to hold the output constant (“Conversion time”)


■ *Goal:*

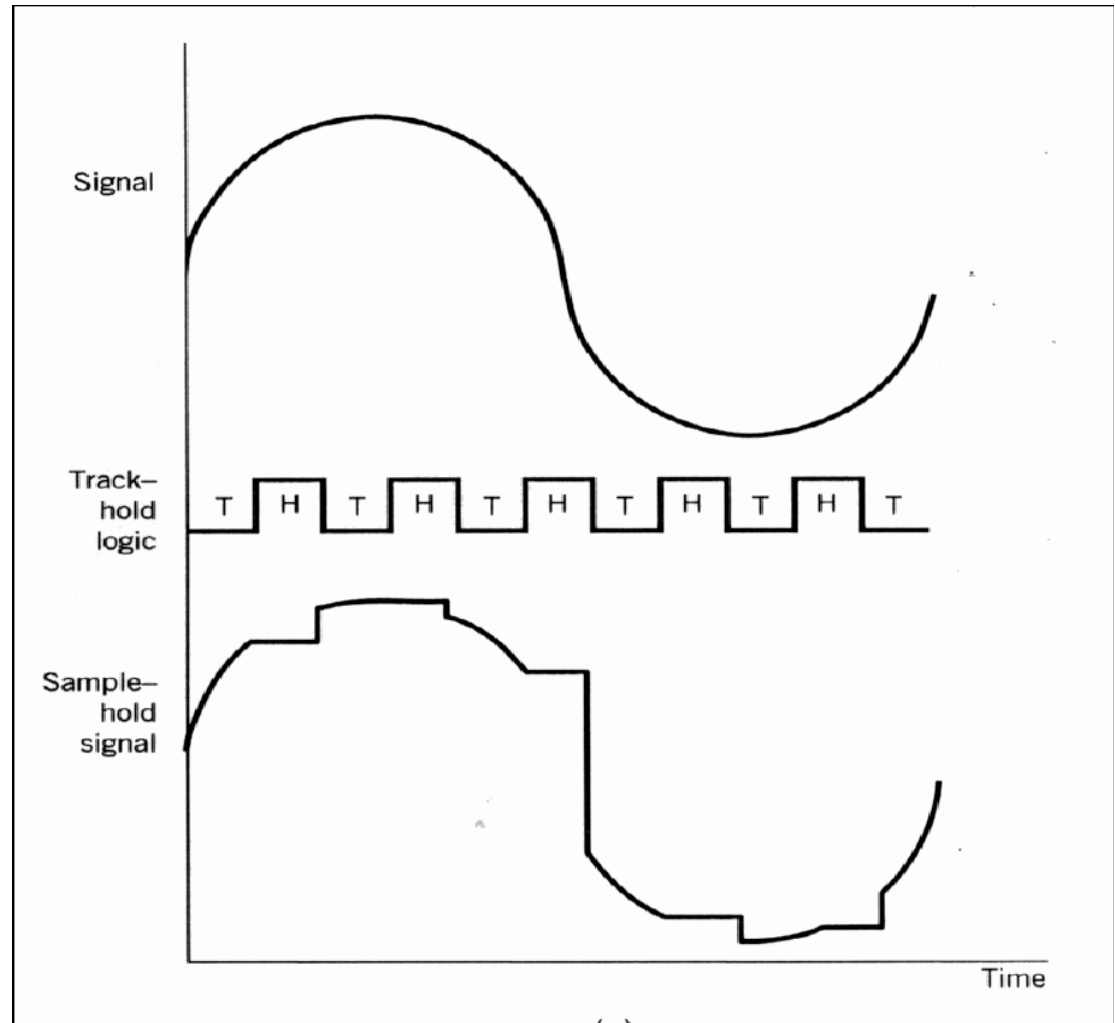- Provide a steady voltage level to the ADC during conversion



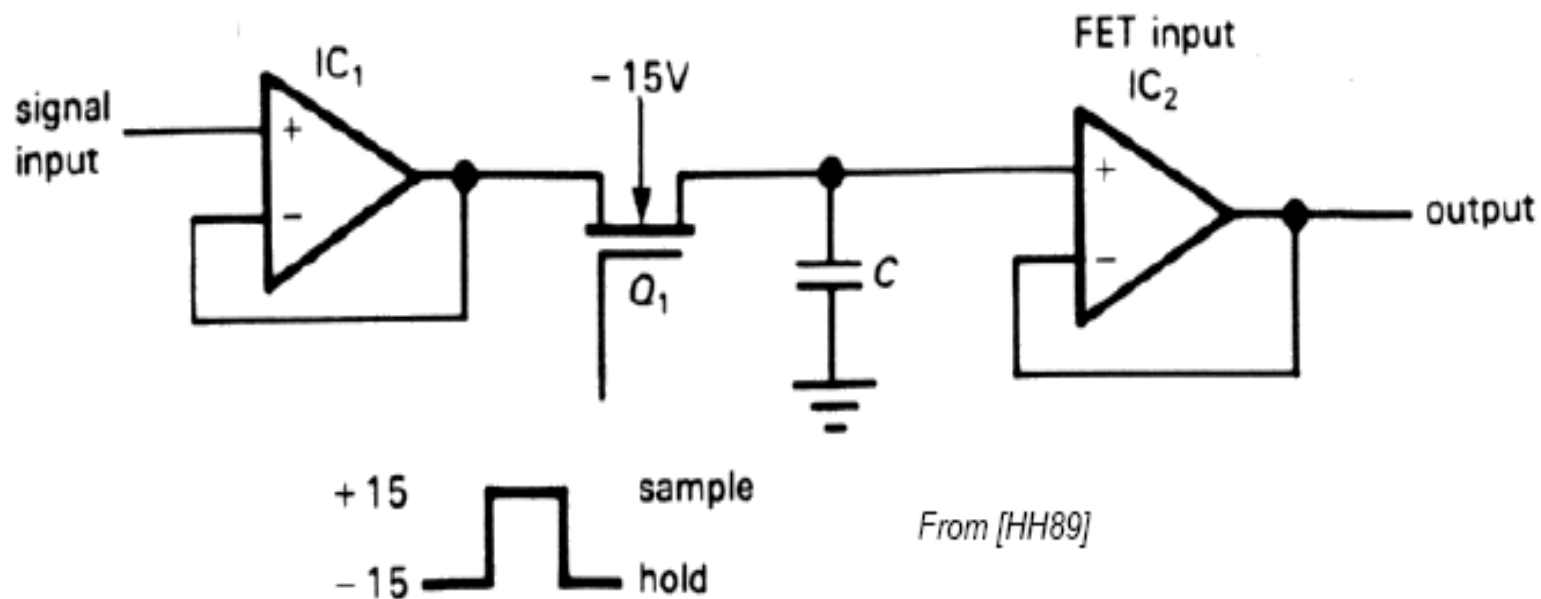Example S/H circuit components


- FET-based switch
- Capacitor to hold voltage steady
- Voltage followers as buffers



Main S/H circuit components

■ Components

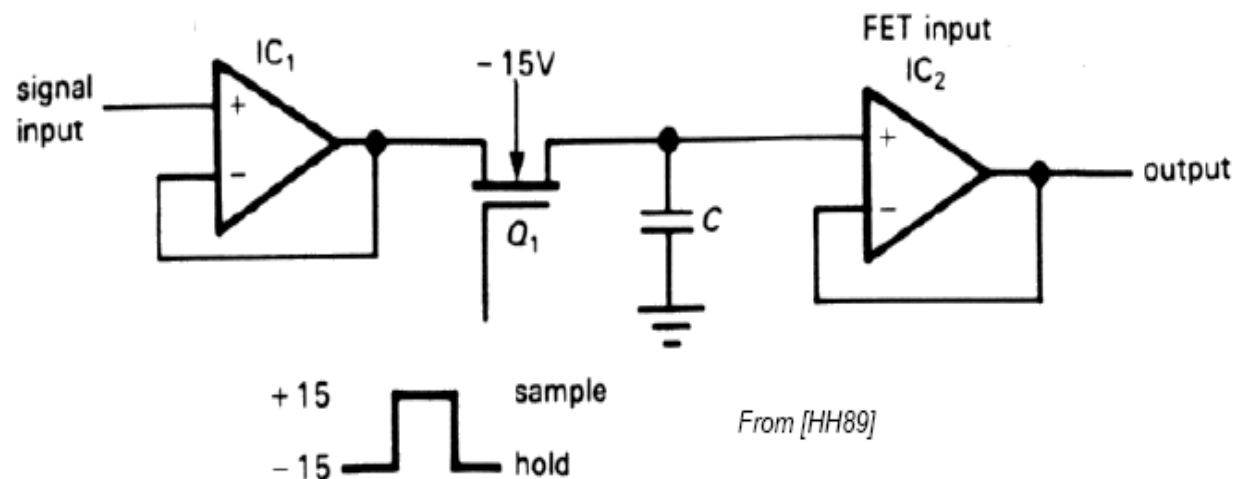- FET-based switch
- Capacitor to hold voltage steady
- Voltage followers as buffers





■ Operation

- IC1 provides low Z_{out} version of input signal
- FET passes the signal during 'sample' and disconnects during 'hold'
- C preserves the value during 'hold'
- IC2 is a high Z_{in} op-amp to minimize capacitor discharge during 'hold'

Multiplexers

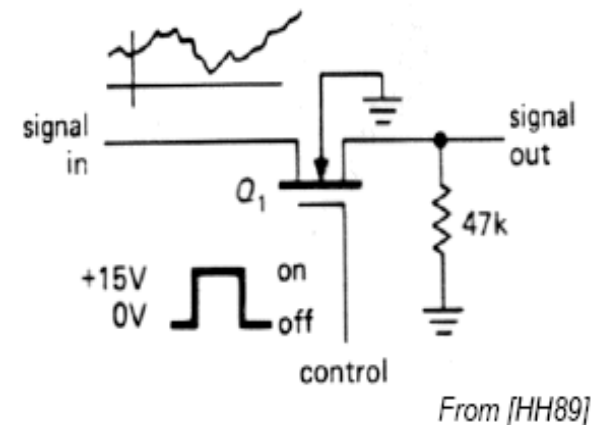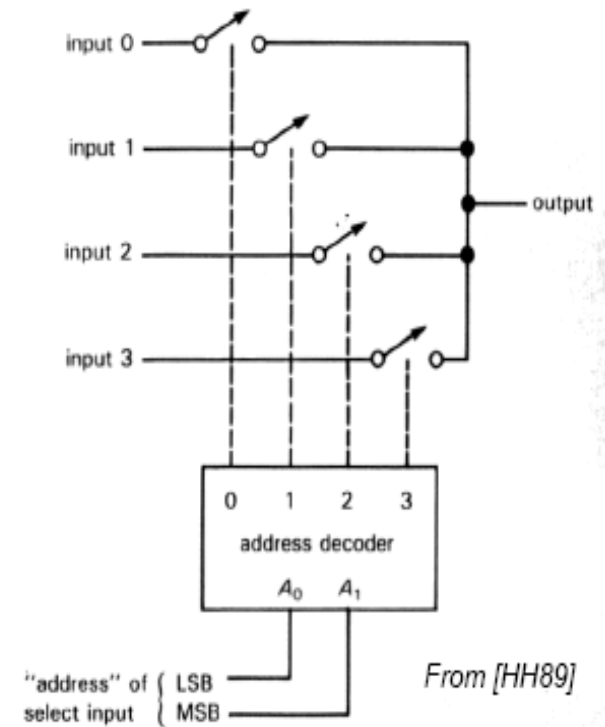- **MUX**: a device that outputs one signal that is selected from several input signals
- **FET-based analog switches**
 - N-channel enhancement-mode MOS-FET
 - When gate is grounded or negative, the FET is nonconducting
 - Drain-source resistance in the order of 10,000 M Ω
 - Bringing the gate to +15V puts the drain-source channel into conduction
 - Drain-source resistance in the order of 100 Ω





Given a stable analog voltage, how to perform A/D conversion?

■ Goal

- **Convert an analog voltage level to a digital value**
- Usually 8 to 16 bits
- Common input range: a few volts,
such as 0 to V_{DD} or -12 V to $+12\text{ V}$

■ Normally use a linear mapping

■ Common concerns

- Resolution
- Accuracy
- Conversion speed

Analog-to-Digital Conversion

■ Typical conversion

$$D = \left(\frac{V_{In} - V_{RefLow}}{V_{RefHigh} - V_{RefLow}} \right) \times 2^n$$

- V_{In} = analog input voltage
- D = binary output value
- n = number of bits
- $V_{RefHigh}$ = upper reference voltage
- V_{RefLow} = lower reference voltage




Methods for A/D conversion

- Flash converter
- Counting converter
- Successive approximation


Flash (parallel) conversion

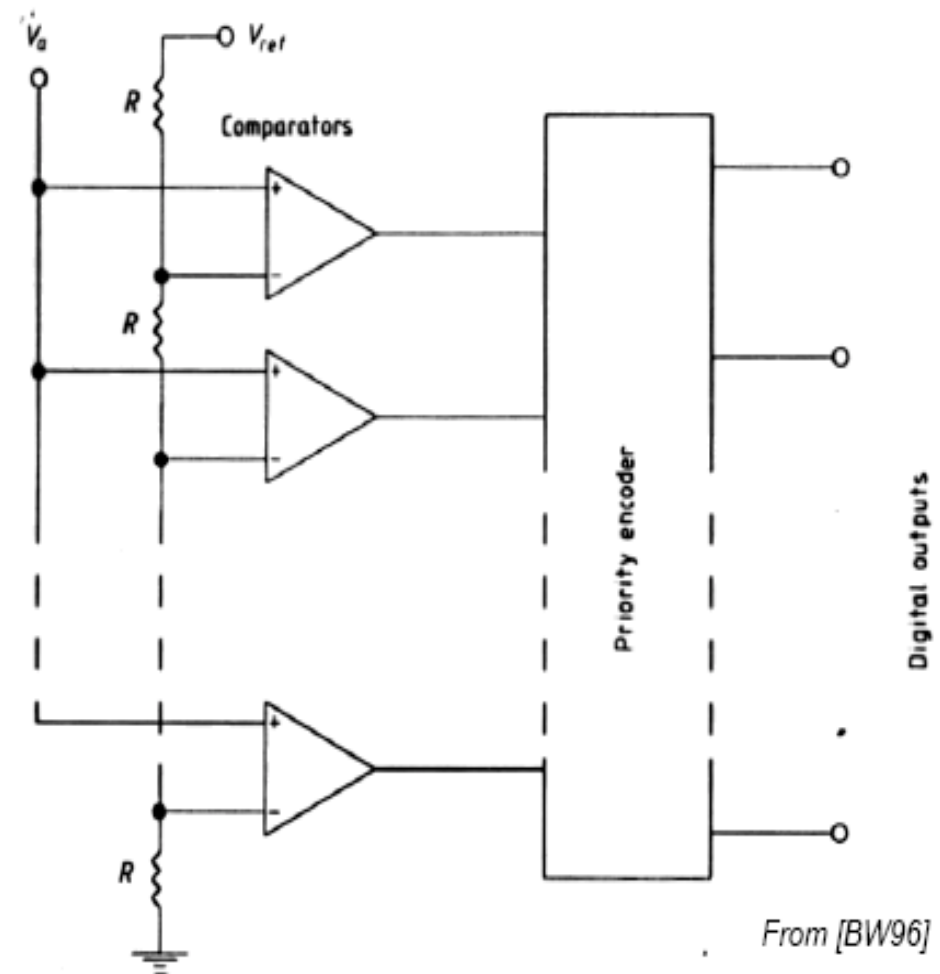- Use 2^n comparators
- Priority encoder
- Fast & *expensive*




Counting conversion

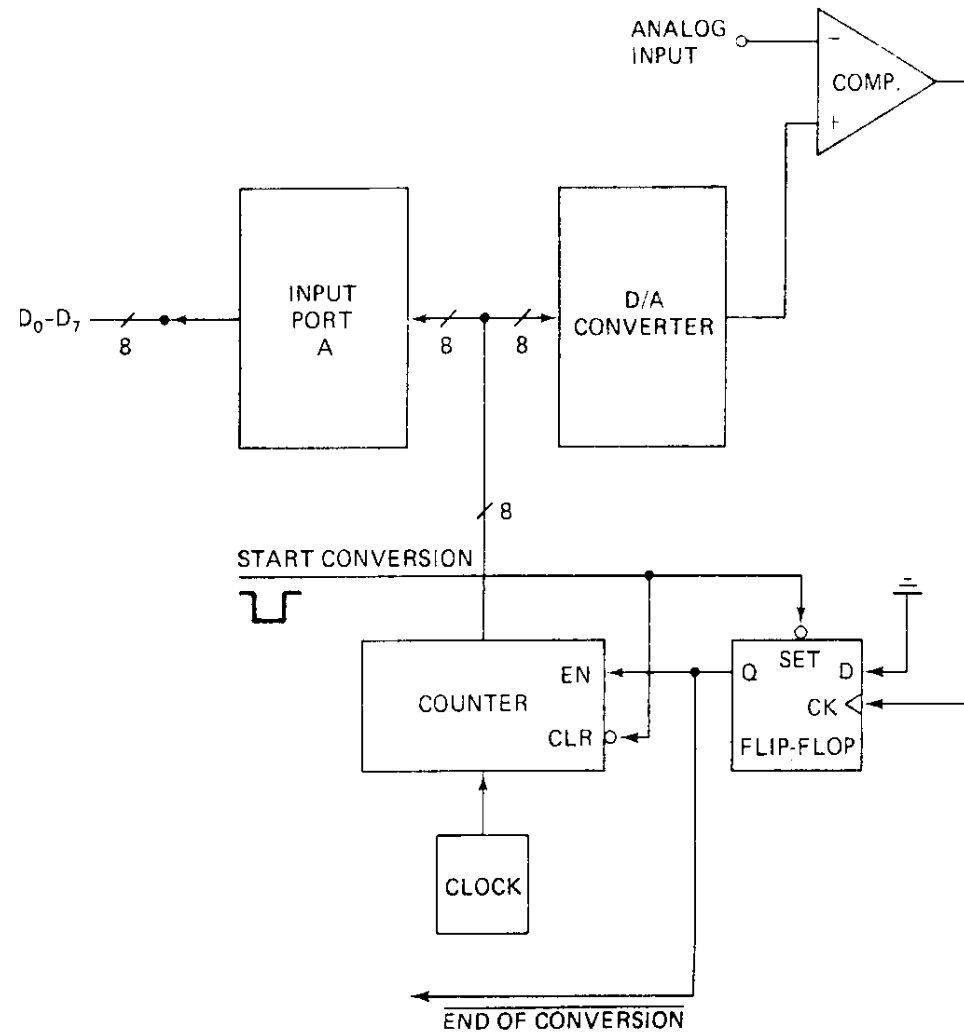- Use a DAC
- Count up until DAC output matches the input voltage
- *Slow*




Successive approximation

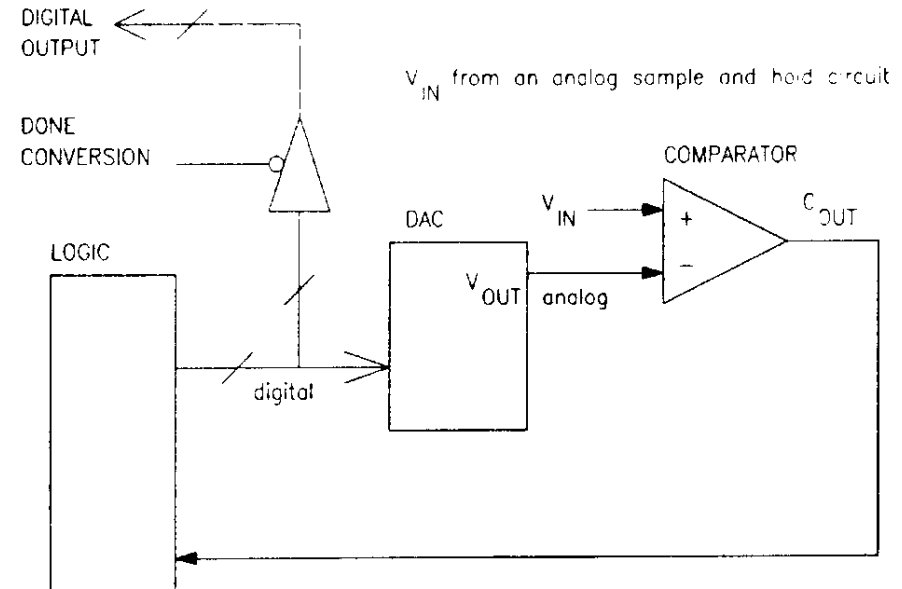- Use a DAC
- Do a *smarter* search for the best digital value



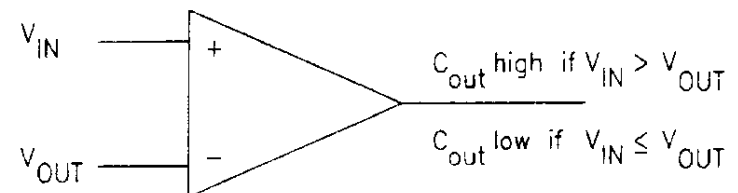
(a) Block Diagram of Successive-Approximation System



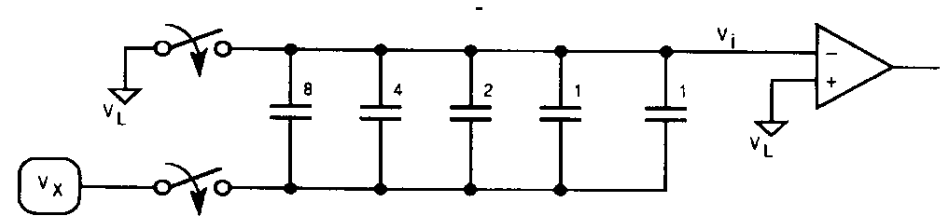
(b) Operation of Comparator

Capacitive ladder


- A form of successive approximation
- First try MSB, then next bit, then next, . . .



(a) Sample Mode

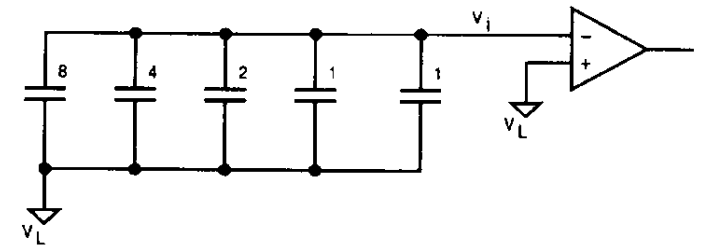

(b) Hold Mode

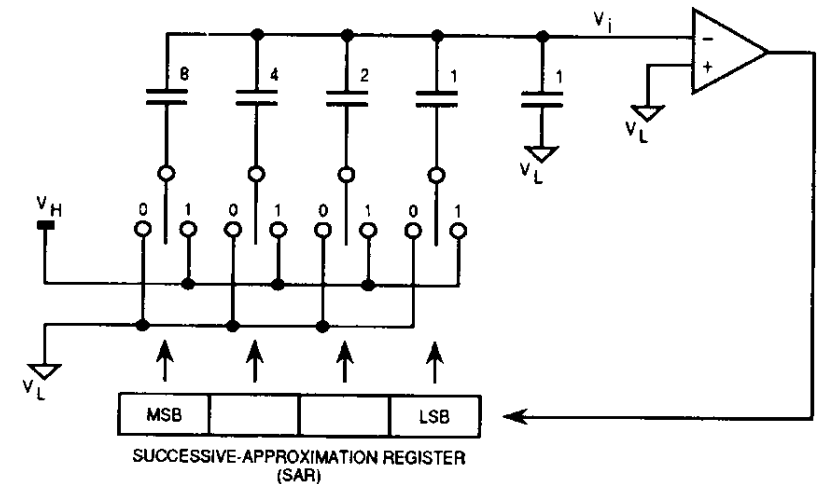

(c) Approximation Mode



Outline

- Motivation
- Basic idea
- ADC on the PIC32
- Digital-to-analog conversion methods
 - Binary weighted ladder
 - R-2R ladder
 - Pulse-width modulation
- Analog-to-digital conversion methods
 - Flash converter
 - Counting converter
 - Successive approximation