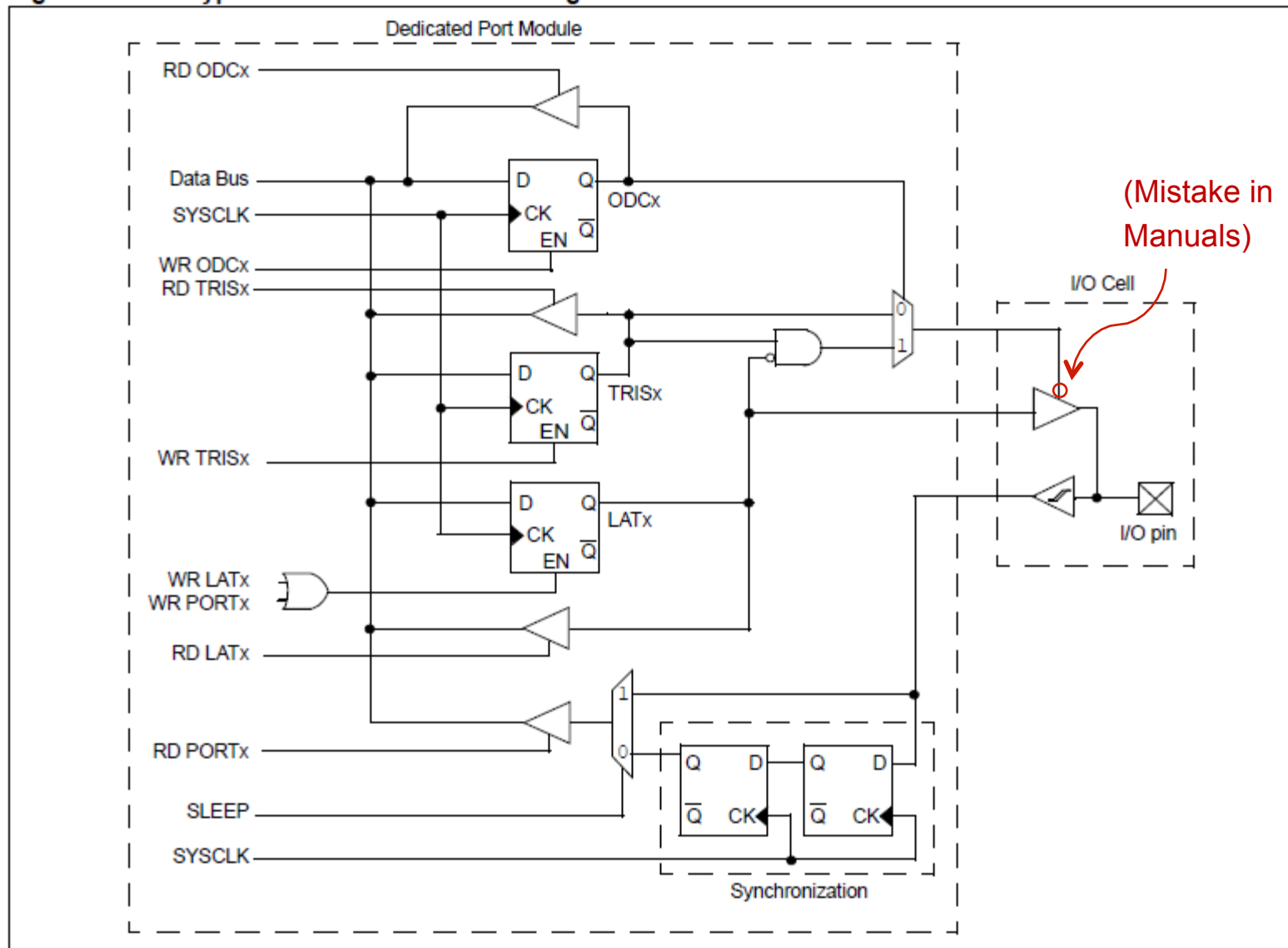


ECE 2534

Interfacing with Switches

One bit on a PIC32 I/O port


Figure 12-1: Typical Port Structure Block Diagram



Timing diagram for an ideal switch



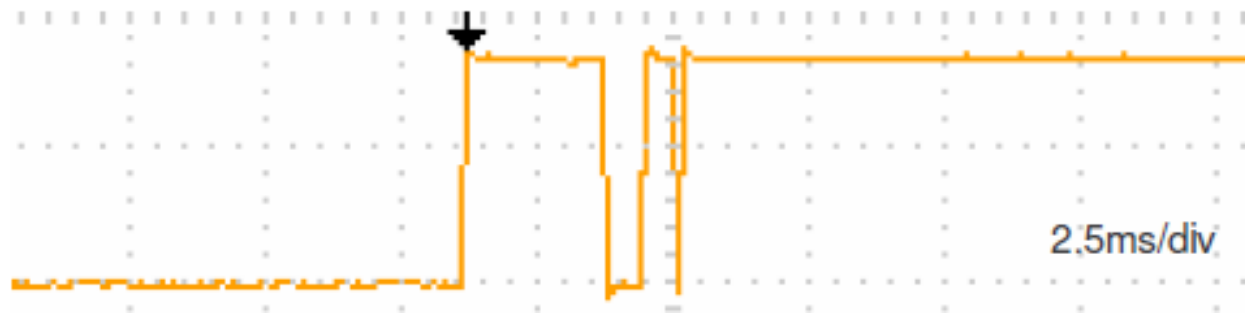Oscilloscope trace from an actual mechanical switch



Summary

- ❑ Most mechanical switches will “bounce” when they are actuated
- ❑ When electrical contacts bounce, noisy and unpredictable electrical signals will result
- ❑ Contact bounce is especially a concern when we want to detect *transitions* of the switch positions
- ❑ These signals need to be **debounced**
 - Do not react to every transition of the electrical signal
 - Instead, use a *delay* to wait for the signal level to stabilize
 - Debouncing can be performed in hardware
 - Debouncing can be performed in software